

# Lecture 17

Wednesday, 4 March 2020 9:47 PM

## Current



$$I = \frac{dq}{dt} \leftarrow \text{amount of charge flowing through a surface in unit time}$$

$$I = \frac{n A dx e}{dt} = ne A v_d \leftarrow \text{drift velocity.}$$

$$\vec{J} = \text{Current Density} = I/A = ne \vec{v}_d$$

Proper definition  $I = \int \vec{J} \cdot d\vec{a}$

Furthermore,  $\frac{\partial \rho}{\partial t} + \nabla \cdot \vec{J} = 0 \leftarrow \text{conservation of charge.}$

for steady state current flow  $\nabla \cdot \vec{J} = 0$

## Ohm's Law

$$\vec{J} = \sigma \vec{E} \Leftrightarrow V = I R \quad \text{where } R = \rho \frac{L}{A}$$

$$\rho = \text{resistivity} = \frac{1}{\sigma}$$

Finally, the power dissipated across any circuit element

$$P = VI$$

for ohmic elements  $\Rightarrow P = I^2 R$

## Circuits

- Charge conservation  $\nabla \cdot \vec{J} = 0$
- Kirchoff's Loop Law
  - Electrostatic Field
  - $\oint \vec{E} \cdot d\vec{s} = 0$



\* In a 6 GeV electron synchrotron, electrons travel around the machine in an approximately circular path 240 meters long. It is normal to have about  $10^{11}$  e<sup>-</sup>s circling on this path during a cycle of acceleration. The speed of the electrons is practically that of light. What is current?

$$\text{No of trips made per second} = \frac{3 \times 10^8 \text{ m/s}}{240} = 1.25 \times 10^6 \text{ s}^{-1}$$


$$\therefore I = \frac{Q}{T} \leftarrow \text{charge through loop per sec} = 1.25 \times 10^6 \times 10^{11} \times 1.6 \times 10^{-19} \text{ A} = 0.02 \text{ A}$$

\* We have  $5 \times 10^{16}$  doubly charged positive ions per  $\text{m}^3$ , all moving west with a speed of  $10^5 \text{ m/s}$ . In the same region there are  $10^{17}$  e<sup>-</sup> per  $\text{m}^3$  moving northeast with a speed of  $10^6 \text{ m/s}$ . What is the magnitude and direction of  $\vec{J}$ ?

$$J_{\text{ion}} = ne v_d = 2e \times 5 \times 10^{16} \times 10^5 = 1.6 \times 10^3 \text{ A/m}^2 \text{ (-i)}$$

$$J_{\text{elec}} = ne v_d = e \times 10^{17} \times 10^6 = -1.6 \times 10^4 \text{ A/m}^2 \text{ (i+j)}$$

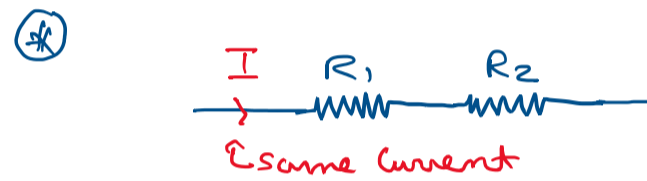
$$\vec{J}_{\text{tot}} = \left\langle -J_{\text{ion}} - \frac{J_{\text{elec}}}{\sqrt{2}}, -\frac{J_{\text{elec}}}{\sqrt{2}} \right\rangle$$



$$V_{\text{tot}} = IR_1 + IR_2 \leftarrow \text{drop in voltage}$$

$$V_{\text{tot}} = I R_{\text{eq}}$$

$$\therefore R_{\text{eq}} = R_1 + R_2$$

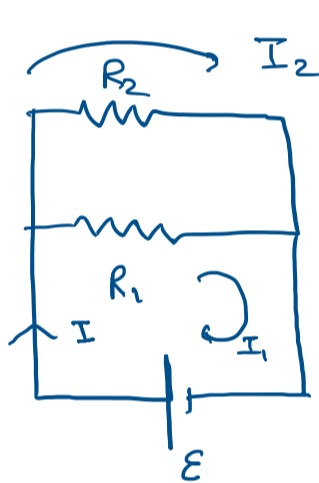

$$E - I_1 R_1 = 0$$

$$I = I_1 + I_2$$


$$-I_2 R_2 + I_1 R_1 = 0$$

$$\Rightarrow I = I_1 + \frac{I_1 R_1}{R_2}$$

$$\Rightarrow I = \frac{E}{R_1} + \frac{E}{R_2}$$

$$\Rightarrow E = I \frac{R_1 R_2}{R_1 + R_2}$$
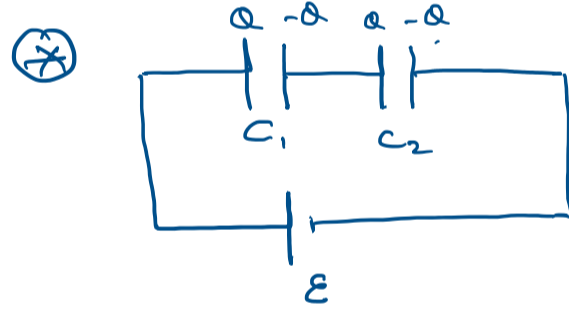
$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$




$$-\frac{Q}{C_1} - \frac{Q}{C_2} + E = 0$$

$$E = Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$

Comparing with  $E = \frac{Q}{C_{\text{eq}}}$

$$\therefore C_{\text{eq}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$= \frac{C_1 C_2}{C_1 + C_2}$$

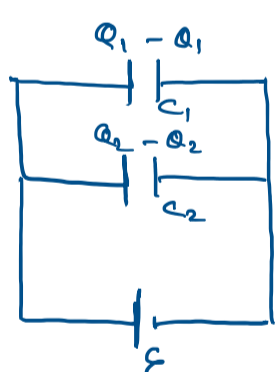

$$E = \frac{Q_1}{C_1}$$


$$Q = Q_1 + Q_2$$

$$-\frac{Q_1}{C_1} + \frac{Q_2}{C_2} = 0$$

$$\Rightarrow Q = Q_1 + Q_1 \frac{C_2}{C_1}$$

$$\Rightarrow Q = EC_1 + EC_2$$

$$\Rightarrow E = \frac{Q}{C_1 + C_2}$$

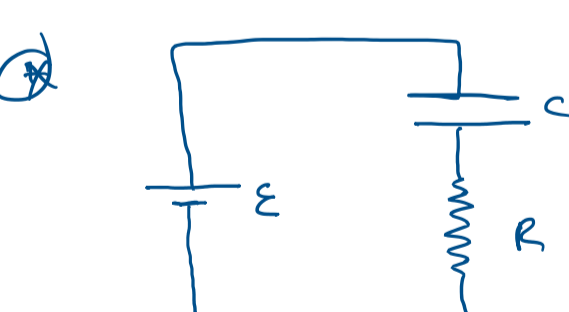

$$0 = E - \frac{Q}{C} - IR$$

$$\Rightarrow \frac{dQ}{dt} = \frac{E}{R} - \frac{Q}{RC}$$



$$\Rightarrow \frac{dQ}{\left( \frac{E}{R} - \frac{Q}{RC} \right)} = dt$$

$$\Rightarrow (-RC) \ln \left( \frac{E/R - Q/RC}{E/R} \right) = t$$

$$\Rightarrow \frac{E}{R} - \frac{Q}{RC} = \frac{E}{R} e^{-t/RC}$$

$$\Rightarrow Q = EC (1 - e^{-t/RC})$$

$$\& I = \frac{E}{R} e^{-t/RC}$$

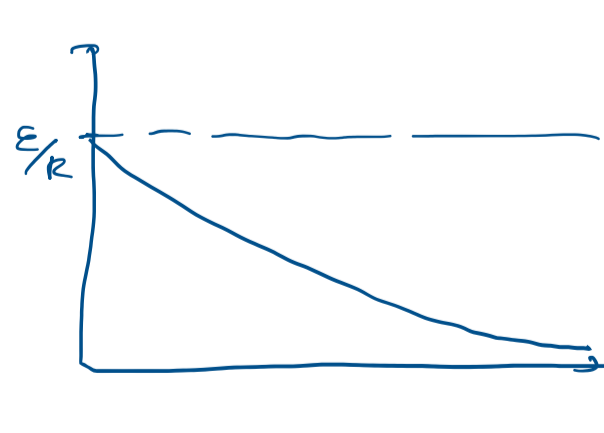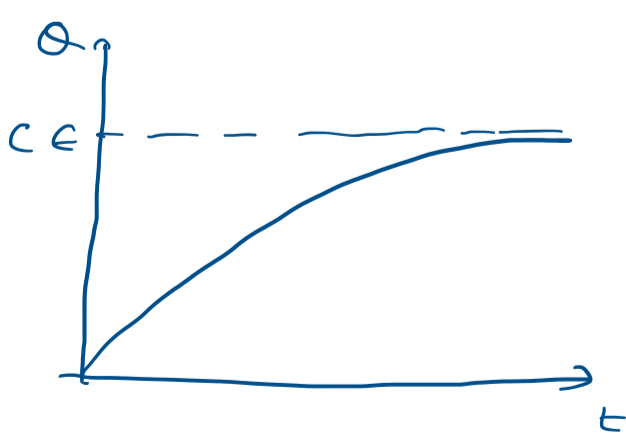

Total energy delivered by battery =  $\int_0^{\infty} E I(t) dt$

$$= \int_0^{Q_0} E dQ$$

$$= E Q_0$$

$$= CE^2$$

$$W_{\text{resistor}} = \int_0^{\infty} I^2(t) R dt$$

$$= \int_0^{\infty} \frac{E^2}{R} e^{-2t/RC} dt$$

$$= \frac{1}{2} RC \frac{E^2}{R} = \frac{1}{2} CE^2$$

$$W_{\text{capacitor}} = \frac{1}{2} \frac{Q_{\text{max}}^2}{C}$$

$$= \frac{1}{2} CE^2$$