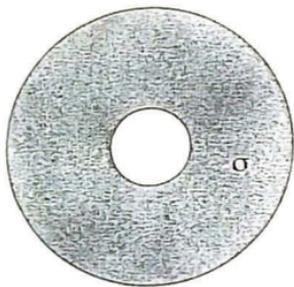



A spherical capacitor consisting of two concentric conductors centered on the origin has capacitance C . The region between the conductors is filled with a material with electrical conductivity σ .



At $t = 0$ the capacitor is charged with a total charge Q_0 on the inner conductor and $-Q_0$ on the outer conductor.

- (2 points) Write an expression for the current density $\vec{J}(r)$ in terms of Q_0 and σ . Use this expression to obtain an expression for the total current I .
- (1 point) Use the result for I from part (a) and Ohm's Law to obtain an expression for the total resistance R between the two conductors in terms of σ and C .
- (1 point) Draw an equivalent circuit for the capacitor/resistor combination.
- (2 points) Write a differential equation for the charge on the capacitor.
- (2 points) Solve for the charge on the capacitor as a function of time in terms of Q_0 and σ .
- (1 point) What is the total energy deposited in the resistive material between the conductors, in terms of Q_0 and C ?
- (1 point) The energy deposited per unit volume varies as a function of radius r between the conductors. Derive an expression for the energy deposited per unit volume \mathcal{E} in terms of Q_0 and the radial coordinate r .

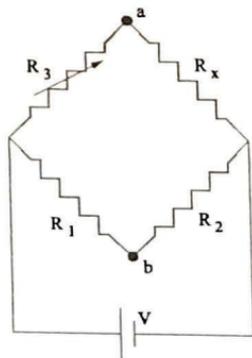A Wheatstone bridge is a device to measure the resistance of an unknown resistor R_x in terms of three known resistances: R_1 , R_2 , and a variable resistor R_3 . Such a device is shown in the diagram below, to which you can refer in answering the following questions.




- (a.) (2 points) What is the voltage V_{ab} between points a and b in terms of the applied voltage V and the 4 resistances?
- (b.) (2 points) The variable resistor R_3 is now adjusted so that $V_{ab} = 0$. Solve for the unknown resistance R_x in terms of the 3 known values R_1 , R_2 , and R_3 .

Assume that $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_3 = 30\Omega$, and $R_x = 60\Omega$. The EMF source (V) is disconnected and a capacitor is connected in its place. The capacitor is initially charged to a voltage of 1000 Volts. The capacitor voltage then decreases to 500 V in a time 10^{-4} seconds after being connected to the circuit. Please give numerical answers to parts (c), (d), and (e) below.

- (c.) (2 points) What is the capacitance C in Farads?
- (d.) (2 points) What is the total energy in Joules that has been dissipated in the resistors during the 10^{-4} second time interval?
- (e.) (2 points) Compute the fraction of the total energy that is deposited in each of the 4 resistors.

Problem 5 – RC circuit

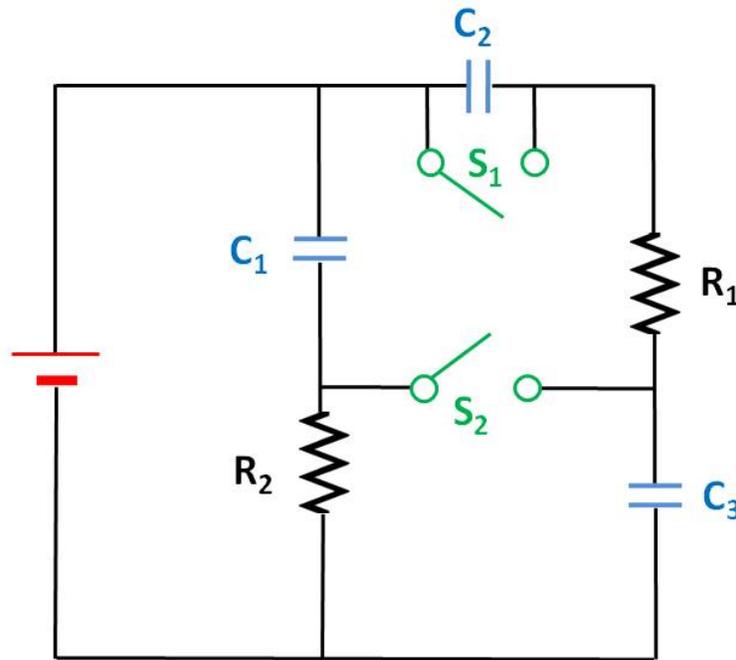


Consider the RC circuit above. After both switches S_1 and S_2 have been closed for a long time, the electric circuit shown above carries a steady time independent current. Take $C_1 = 2 \mu\text{F}$, $C_2 = 6 \mu\text{F}$, $C_3 = 4 \mu\text{F}$, $R_1 = 2 \text{ k}\Omega$ and $R_2 = 9 \text{ k}\Omega$. The power delivered to R_1 is measured to be 4 W.

- Find the current through the circuit. [1pt]
- Find the charges on C_1 , C_2 and C_3 . [2pts]
- Find the battery voltage. [1pt]
- The switch S_2 is now opened. How long does it take the current through R_1 to decrease to $1/e$ of its initial value? [2pts]
- After waiting a long time such that no currents flow through the circuit anymore the switch S_1 is also opened. What are the new charges across C_1 , C_2 and C_3 after the circuit has reached its new equilibrium? [2pts]

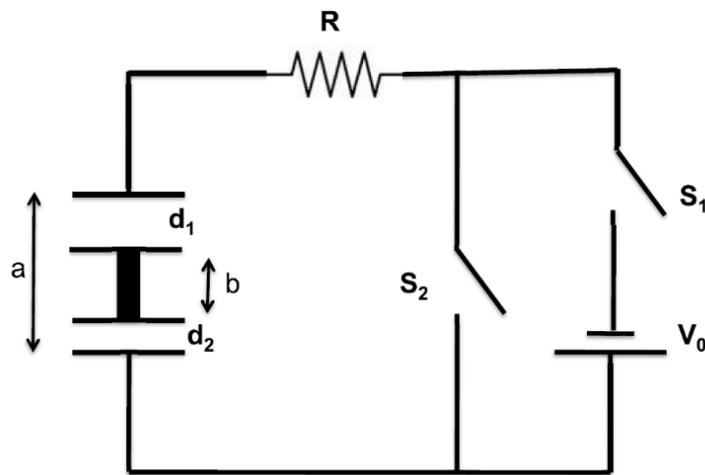Problem 4

The figure below shows two capacitors in series, connected to a resistor R and a battery. The center conductor of length b is movable vertically so that the spacings d_1 and d_2 can be varied within the gap 'a' of the outer plates. The area (A) of each capacitor plate is the same. Initially, the switch S_1 is closed and S_2 open in order to bring the potential difference of the outer capacitor plates to V_0 .

Express your answers to the following questions in terms of the variables given in the problem statement above.



- Find an expression for the capacitance C of the series combination of the two capacitors and show that it is independent of position of the center conductor. [2pts]
- What is the charge density σ on the top plate when the capacitor is fully charged? [2pts]
- What is the change in the energy stored in the capacitor if the center section is removed? [2pts]
- Suppose that at the instant the center section is removed, we also remove the battery by opening S_1 and closing S_2 . How long does it take for the voltage on the outer capacitor plates to drop to $V_0/2$? [2pts]



Solution: From Gauss's law, we know that, at $t = 0$, in the region between the conductors the electric field is

$$\vec{E}(\tau) = \frac{Q_0}{r^2} \hat{r}.$$

From Ohm's Law:

$$\vec{J}(\tau) = \sigma \vec{E}(\tau) = \frac{\sigma Q_0}{r^2} \hat{r}.$$

To find the current we may integrate the flux of \vec{J} through any spherical surface between the conductors:

$$I = \oint \vec{J} \cdot d\vec{a} = 4\pi r^2 \frac{\sigma Q_0}{r^2} = 4\pi \sigma Q_0.$$

- (b) (1 point) Use the result for I from part (a) and Ohm's Law to obtain an expression for the total resistance R between the two conductors in terms of σ and C .

Solution: By Ohm's Law, $R = V/I$, where V is the difference in the electric potential φ between the conductors in the capacitor. By the definition of the capacitance, $V = Q/C$. Therefore:

$$R = \frac{Q_0}{C} \cdot \frac{1}{4\pi Q_0 \sigma} = \frac{1}{4\pi \sigma C}.$$

- (c) (1 point) Draw an equivalent circuit for the capacitor/resistor combination.

Solution: See Figure 4.

- (d) (2 points) Write a differential equation for the charge on the capacitor.

Solution: By Ohm's Law and the definition of the capacitance:

$$IR = V = \frac{Q}{C},$$

where I is the current through the resistor. This current must be equal to minus the time derivative of the charge Q stored in the capacitor. Therefore:

$$-\frac{dQ}{dt} = \frac{Q}{RC} = 4\pi \sigma Q,$$

with the initial condition that $Q(t = 0) = Q_0$.

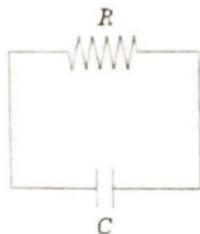


Figure 4: The system is equivalent to a resistance R and a capacitance C connected together. The capacitor will discharge through the resistor.

- (e) (2 points) Solve for the charge on the capacitor as a function of time in terms of Q_0 and σ .

Solution: As explained in Chapter 4 of the textbook, the solution is

$$Q(t) = Q_0 e^{-4\pi\sigma t}.$$

- (f) (1 point) What is the total energy deposited in the resistive material between the conductors, in terms of Q_0 and C ?

Solution: As discussed in chapter 3 of the text:

$$U = \frac{1}{2} C V_0^2 = \frac{Q_0^2}{2C}.$$

- (g) (1 point) The energy deposited per unit volume varies as a function of radius r between the conductors. Derive an expression for the energy deposited per unit volume \mathcal{E} in terms of Q_0 and the radial coordinate r .

Solution: Consider a spherical shell of resistive material, with radius r and thickness δr . From part (a) we know that the current passing through it must be $I(t) = 4\pi\sigma Q(t)$. The resistance of the shell is inversely proportional to the conductance σ , inversely proportional to the cross-section $A = 4\pi r^2$, and proportional to the thickness δr . That is:

$$R = \frac{\delta r}{4\pi r^2 \sigma}.$$

The energy per unit time (power) dissipated by the resistive shell is

$$P(t) = \frac{dU}{dt} = I^2(t) R = [4\pi\sigma Q(t)]^2 \cdot \left(\frac{\delta r}{4\pi r^2 \sigma} \right) = \frac{4\pi\sigma Q^2(t) \delta r}{r^2},$$

which implies that the total energy dissipated during the discharge is:

$$U = \int_0^\infty dt \frac{4\pi\sigma Q^2(t) \delta r}{r^2}.$$

To obtain the energy volume density \mathcal{E} we simply divide this by the volume of the spherical shell $V = 4\pi r^2 \delta r$, which gives

$$\mathcal{E} = \int_0^\infty dt \frac{\sigma Q^2(t)}{r^4}.$$

Now we may plug in the result for $Q(t)$ from part (e). The integration then gives:

$$\mathcal{E} = \frac{\sigma Q_0^2}{r^4} \int_0^\infty dt e^{-8\pi\sigma t} = \frac{\sigma Q_0^2}{r^4} \frac{-1}{8\pi\sigma} [e^{-8\pi\sigma t}]_0^\infty = \frac{Q_0^2}{8\pi r^4}.$$

Another solution to this problem relies on the observation that, since no energy flows radially during the discharge, all of the energy deposited in a given shell of radius r must have originally been contained in that shell's electrostatic field. The volume density of the energy stored in any electrostatic field is:

$$\mathcal{E} = \frac{1}{8\pi} E^2.$$

Inside the capacitor the electric field is initially given by:

$$\vec{E}(r) = \frac{Q_0}{r^2} \hat{r},$$


which implies that

$$E^2(r) = \vec{E}(r) \cdot \vec{E}(r) = \frac{Q_0^2}{r^4}.$$

Therefore:

$$\mathcal{E} = \frac{Q_0^2}{8\pi r^4}.$$

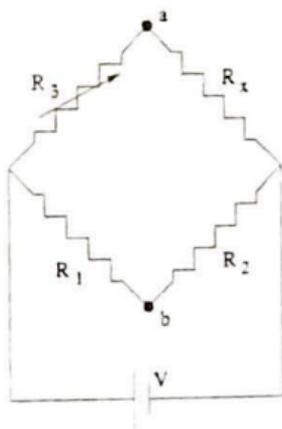A Wheatstone bridge is a device to measure the resistance of an unknown resistor R_x in terms of three known resistances: R_1 , R_2 , and a variable resistor R_3 . Such a device is shown in the diagram below, to which you can refer in answering the following questions.



- (a) (2 points) What is the voltage V_{ab} between points a and b in terms of the applied voltage V and the 4 resistances?

Solution: Applying Ohm's law to each branch, we find the currents I_{12} and I_{3x} .

$$\begin{aligned}
 V &= IR_{\text{eff}} \\
 I_{12} &= \frac{V}{R_1 + R_2} \quad \text{and} \quad I_{3x} = \frac{V}{R_3 + R_x} \\
 V_{ab} &= V_a - V_b \\
 &= (V - \Delta V_3) - (V - \Delta V_1) \\
 &= \Delta V_1 - \Delta V_3 \\
 &= I_{12}R_1 - I_{3x}R_3 \\
 &= V \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_x} \right)
 \end{aligned}$$

- (b) (2 points) The variable resistor R_3 is now adjusted so that $V_{ab} = 0$. Solve for the unknown resistance R_x in terms of the 3 known values R_1 , R_2 , and R_3 .

Solution:

$$\begin{aligned}
 V_{ab} &= 0 \\
 \Rightarrow \frac{R_1}{R_1 + R_2} &= \frac{R_3}{R_3 + R_x} \\
 R_x &= \frac{R_2 R_3}{R_1}
 \end{aligned}$$

Assume that $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_3 = 30\Omega$, and $R_x = 60\Omega$. The EMF source (V) is disconnected and a capacitor is connected in its place. The capacitor is initially charged to a voltage of 1000 Volts. The capacitor voltage then decreases to 500 V in a time 10^{-4} seconds after being connected to the circuit. Please give numerical

Solution: First we find the R_{eff} for the circuit. Using the series and parallel addition rules, we get:

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_x}$$
$$R_{\text{eff}} = 22.5 \Omega$$

Since we know the solution to the RC circuit, we know the voltage obeys

$$V(t) = V_0 e^{-t_1/(RC)}$$

Given we know the time t_1 for the voltage to drop by half, we solve for C .

$$\frac{1}{2} = e^{-t_1/(RC)}$$
$$C = \frac{t_1}{R \ln 2} = \underline{6.4 \times 10^{-6} \text{ F}}$$

- (d) (2 points) What is the total energy in Joules that has been dissipated in the resistors during the 10^{-4} second time interval?

Solution: All the energy lost in resistors has come from the energy stored in the capacitor.

$$U_{\text{lost}} = U_i - U_f = \frac{1}{2} CV_0^2 - \frac{1}{2} CV(t_1)^2$$
$$= \frac{1}{2} CV_0^2 \left(1 - \frac{1}{4} \right)$$
$$= \underline{\frac{3}{8} CV_0^2 = 2.4 \text{ J}}$$

- (e) (2 points) Compute the fraction of the total energy that is deposited in each of the 4 resistors.

Solution: Since the potential difference across the branch 12 and $3x$ is always the same no matter how it drops with time, we know about the energy dissipated ratio E_{12}/E_{3x} from $P = V^2/R$,

$$\frac{E_{12}}{E_{3x}} = \frac{R_{3x}}{R_{12}}$$
$$= \frac{30 + 60}{10 + 20}$$
$$= 3$$

Similarly by considering branch 12 and branch 3x individually with $P = I^2R$,

$$\begin{aligned}\frac{E_2}{E_1} &= \frac{I_{12}^2 R_2}{I_{12}^2 R_1} \\ &= \frac{R_2}{R_1} \\ &= 2\end{aligned}$$

$$\begin{aligned}\frac{E_x}{E_3} &= \frac{I_{3x}^2 R_x}{I_{3x}^2 R_3} \\ &= \frac{R_x}{R_3} \\ &= 2\end{aligned}$$

Therefore, we can compute the fraction of the total energy deposited,

$$\left(\frac{E_1}{E_{\text{total}}}, \frac{E_2}{E_{\text{total}}}, \frac{E_3}{E_{\text{total}}}, \frac{E_x}{E_{\text{total}}} \right) = \left(\frac{3}{12}, \frac{6}{12}, \frac{1}{12}, \frac{2}{12} \right)$$

Problem 5 Solution:

a) If the current is time independent the charges on the capacitors are constant and no current flows to them. We can then forget about the capacitors for a second and consider the circuit consisting only of the EMF going to S1 to R1 to S2 to R2 and back to the EMF. A constant current I flows through this circuit. The power across the 1st resistor is 4W. We can deduce that

$$P = IV = I^2R = I^2 * (2 * 10^3) \rightarrow I = \sqrt{\frac{4}{2 * 10^3}} = .045A. \quad (1)$$

b) Denote the charges on the three capacitors Q_1, Q_2, Q_3 . We can use Kirchoff loops to calculate the charge on each capacitor. S1 is closed so the kirchoff loop around S1 and C2 implies no charge can exist on C2 since $V_2 = \frac{Q_2}{C_2} = 0$. So

$$Q_2 = 0. \quad (2)$$

Making a Kirchoff loop around C_1, C_2 and R_1 gives

$$\frac{Q_1}{C_1} - IR_1 = 0 \quad (3)$$

which implies

$$Q_1 = IC_1R_1 = .045(2 * 10^{-6})(2 * 10^3) = 1.79 * 10^{-4}C. \quad (4)$$

To find Q_3 we make a kirchoff loop around the lower box. Following the procedure for Q_1 we get

$$Q_3 = IC_3R_2 = .045(4 * 10^{-6})(9 * 10^3) = 1.609 * 10^{-3}C. \quad (5)$$

c) Denote the emf voltage by ϵ . We can make a loop following the current path to get

$$\epsilon - IR_1 - IR_2 = 0 \rightarrow \epsilon = I(R_1 + R_2) = .045 * (2 + 9) * 10^3 = 491.7V. \quad (6)$$

d) Note that if S2 is open all of the current passing through R_1 has to pass either to or from C_3 . We can then formulate a differential equation for this current using Kirchoff's loop law:

$$\epsilon - iR_1 - \frac{Q}{C_3} = 0 \quad (7)$$

where the current $i = \frac{dQ}{dt}$ is now time dependent. Differentiating 7 we find

$$\frac{di}{dt} = -\frac{i}{R_1 C_3}. \quad (8)$$

The solutions to this is

$$i = i_0 e^{-\frac{t}{R_1 C_3}} \quad (9)$$

where $i_0 = I$ from part a). We can immediately see that at time

$$t = R_1 C_3 = (2 * 10^3) * (4 * 10^{-6}) = 8 * 10^{-3} s \quad (10)$$

the current reduces to $\frac{1}{e}$ of its original value.

e) We can calculate the charge on C_3 before S1 is opened by making a kirchoff loop passing from the EMF to R1 to C_3 and back to the EMF:

$$\epsilon - (0) * R_1 - \frac{Q_3}{C_3} = 0 \rightarrow Q_3 = \epsilon C_3 = 491.7 * 4 * 10^{-6} = 1.9668 * 10^{-3} C. \quad (11)$$

If no current is flowing between C_2 and C_3 the resistor plays no role and can be eliminated from the analysis. By Kirchoff's loop law

$$\epsilon - \frac{Q_2}{C_2} - \frac{Q_3}{C_3} = 0. \quad (12)$$

This implies

$$\frac{Q_2}{6 * 10^{-6}} + \frac{Q_3}{4 * 10^{-6}} = 491.7. \quad (13)$$

Note that when S1 is opened the total charge that is on the negative plate of C_2 and the positive plate of C_3 has to sum to the charge on the positive plate of C_3 right before S1 was flipped by charge conservation (now that the switch is flipped, the charge has nowhere else to go). We then have

$$-Q_2 + Q_3 = 1.9668 * 10^{-3}. \quad (14)$$

This system of equations can be solved to find

$$Q_2 = 0 \text{ and } Q_3 = 1.967 * 10^{-3} C. \quad (15)$$

The charge across C_1 is easy to find by realizing the current through R_2 is zero and by using a Kirchoff loop:

$$Q_1 = C_1 V_1 = C_1 * \epsilon = 2 * 10^{-6} * 491.7 = 9.834 * 10^{-4} C. \quad (16)$$