

Lecture 11

⊛ Why even study the $e^{i\omega t}$ method if it can only solve for sinusoidally varying sources?

→ All sources can be Fourier expanded in terms of sine functions

⊛ Kirchoff's Law of Current

→ Just like voltage law, conservation of charge must also hold \therefore at all functions $\sum I_i(t) = 0$

Power for AC circuits

$$P = VI$$

$$= E_0 \cos(\omega t) \frac{E_0}{|Z|} \cos(\omega t + \phi)$$


$$= \frac{E_0^2}{|Z|} (\cos^2(\omega t) \cos \phi - \cos(\omega t) \sin(\omega t) \cos \phi)$$

$$\bar{P} = \frac{E_0^2}{2|Z|} \cos \phi$$

$$\text{Now, } \frac{E_0}{\sqrt{2}} = E_{\text{rms}} \text{ \& } \frac{I_0}{\sqrt{2}} = I_{\text{rms}}$$

$$\therefore \bar{P} = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$= V_{\text{rms}} I_{\text{rms}} \left| \frac{R}{Z} \right|$$

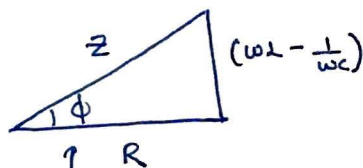

Use phasor diagram to understand this

Only the resistors dissipate any energy. L & C do not dissipate any energy.

⊛ Calculate the equivalent power factor for parallel RLC circuit.

$$Z = \frac{1}{\frac{1}{R} + i(\omega C - \frac{1}{\omega L})} = \frac{Y_R - i(\omega C - \frac{1}{\omega L})}{(Y_R)^2 + (\omega C - \frac{1}{\omega L})^2}$$


$$\left| \frac{1}{Z} \right| = \frac{1}{\sqrt{(Y_R)^2 + (\omega C - \frac{1}{\omega L})^2}} \left(\frac{Y_R}{Y_{Z\text{mag}}} - \frac{i(\omega C - \frac{1}{\omega L})}{Y_{Z\text{mag}}} \right)$$

$$\cos \phi = \frac{Y_R}{\sqrt{(Y_R)^2 + (\omega C - \frac{1}{\omega L})^2}}$$

$$\therefore \bar{P} = \frac{1}{2} \epsilon_0 \frac{\epsilon_0}{Z} \frac{Y_R}{\frac{1}{2}} = \frac{\epsilon_0^2}{2R}$$

↳ Only the resistance contributes to the power dissipation in the circuit

Problem 1

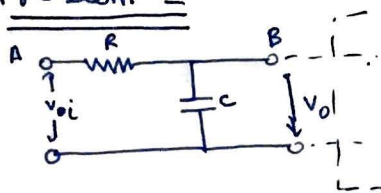

An AC source of $v_{oi} \cos(\omega t)$ is applied across terminals A. B is connected to a very high impedance.

- i) Calculate $|v_o/v_{oi}|^2$
- ii) Choose R & C to make this ratio 0.1 for 5000 Hz signal. Interpret this.
- iii) Show that at high frequency, signal power is reduced by $1/4$ for every doubling of frequency.
- iv) How do you make it $1/16$ for every such doubling.

$$i) \tilde{v} = v_{oi} e^{i\omega t}$$

$$\tilde{I}_C = \tilde{v}/Z = \frac{\tilde{v}}{R + \frac{1}{i\omega C}} = \frac{\tilde{v}}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} e^{i \tan^{-1}(\frac{1}{\omega CR})}$$

$$\tilde{v}_C = \frac{\tilde{v}}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \frac{1}{i\omega C} e^{i \tan^{-1}(\frac{1}{\omega CR})}$$

$$= \frac{\tilde{v}}{\sqrt{1 + (\omega CR)^2}} e^{i \tan^{-1}(\frac{1}{\omega CR} - \pi/2)}$$


$$\therefore |v_o/v_{oi}|^2 = \frac{1}{1 + R^2 \omega^2 C^2}$$

b) $\frac{1}{1 + \omega^2 R^2 C^2} = 0.1 \Rightarrow \omega^2 R^2 C^2 = 9 \Rightarrow RC = \frac{3}{\omega} = 6 \times 10^{-4} \text{ s}$


↑
Choose your combo

c) $\left| \frac{V_o}{V_i} \right|^2 = \frac{1}{\omega^2 R^2 C^2}$ (every doubling of frequency reduces the energy by a factor of 4)
 ↑ at high frequency

d) Just add another loop.

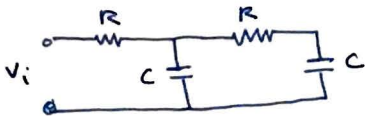

Problem 2

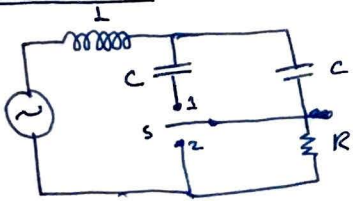

The AC current generator supplies $V(t) = V_0 \cos(\omega t)$. The current through the Resistor can be shown to be $I(t) = I_0 \cos(\omega t + \phi)$, where I_0 and ϕ depend on the position of the switch.

- a) Assume the ω can be varied, V_0 is fixed. Find, when the switch is in position 1, find the value of the angular frequency ω_0 such that the current through the resistor is maximum.
- b) What is the peak current when $\omega = \omega_0$?

The generator, which supplies an rms voltage of 220 V, is now set to a frequency $\nu = 50 \text{ Hz}$. When the switch is open, the current leads the generator voltage by phase $\phi = 45^\circ$. In position 1, the current I lags the voltage by $\phi = -26.6^\circ$. In position 2, the $I_{\text{rms}} = 2 \text{ A}$.

c) Find the values R, L, C .

$$a) Z = R + i \left(\omega L - \frac{1}{2\omega C} \right) = \sqrt{R^2 + \left(\omega L - \frac{1}{2\omega C} \right)^2} e^{i \tan^{-1} \left(\frac{\omega L - 1/\omega C}{R} \right)}$$

Current is maximum when Z is minimum i.e.

$$\omega_0 L = \frac{1}{2\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{2LC}}$$

$$b) I_{\max} = V_0/R = \sqrt{2} V_{\text{rms}}/R$$

$$c) f = 50 \text{ Hz} \Rightarrow \omega = 2\pi f = 100\pi \text{ s}^{-1}$$

Open Switch (series RLC circuit)

$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

↑
Voltage
leads current

$$\Rightarrow \tan(-45^\circ) = \omega L - 1/\omega C / R$$

$$\Rightarrow 1 = \frac{1/\omega C - \omega L}{R} \quad \dots (1)$$

Position 1 (series RL (2C) circuit)

$$\tan \phi = \frac{\omega L - \frac{1}{2\omega C}}{R}$$

$$\Rightarrow \tan(26.6^\circ) = \frac{\omega L - \frac{1}{2\omega C}}{R}$$

$$\Rightarrow \frac{1}{2} = \frac{\omega L - \frac{1}{2\omega C}}{R} \quad \dots (1)$$

$$[i] + [ii] \Rightarrow \frac{3}{2} = \frac{1}{2\omega C R} \Rightarrow R = \frac{1}{3\omega C}$$

$$[i] + 2[ii] \Rightarrow 2 = \frac{\omega L}{R} \Rightarrow R = \omega L/2$$

Position 2

$$I_{\text{rms}} = V_{\text{rms}}/|Z| = V_{\text{rms}}/|\omega L - \frac{1}{\omega C}| = V_{\text{rms}}/R$$

$$\therefore 2 = 220/R \Rightarrow R = 110 \Omega$$

$$C = 9.65 \mu\text{F} ; L = 0.7 \text{ H}$$

Problem 3

Loop Antenna: An EM wave propagating in air has a magnetic field given by.

$$B_x = 0, B_y = 0, B_z = B_0 \cos(\omega t - kx)$$

It encounters a circular loop antenna of radius a centered at the origin & lying in xy plane. The radius of antenna $a \ll \lambda$ where λ is the wavelength of the wave.

→ Try interpreting this.

a) Find $\Phi_{\text{mag}}(t) = \int \vec{B} \cdot d\vec{a}$ through the loop antenna.

✓
The loop has a self inductance L and resistance R .

$$\therefore IR = -L \frac{dI}{dt} - \frac{d\Phi_{\text{mag}}}{dt}$$

b) Assume a solution of the form $I(t) = I_0 \sin(\omega t - \phi)$ where ω is the angular frequency of the EM wave, I_0 is the amplitude and ϕ is the phase shift between changing magnetic flux & current. Find ϕ & I_0 .

c) What is the magnetic field at the center of the loop by current $I(t)$?

a) $\Phi_{\text{mag}} = B_0 \cos(\omega t - kx) \pi a^2 = B_0 \pi a^2 \cos(\omega t)$
(You can consider B_0 at the center of the loop as $\lambda \ll a$)

b)

$$\frac{d\Phi_{\text{mag}}}{dt} = -IR - L \frac{dI}{dt}$$

$$\Rightarrow B_0 \pi a^2 \omega \sin(\omega t) = IR + L \frac{dI}{dt}$$

$$\Rightarrow B_0 \pi a^2 \omega \sin(\omega t) = IR + L \frac{dI}{dt}$$

$$Z = R + i\omega L = \sqrt{R^2 + (\omega L)^2} e^{i \tan^{-1}(\omega L/R)}$$

$$\text{let } v = v_0 e^{i(\omega t - \pi/2)}$$

$$\therefore \tilde{I} = \frac{\tilde{V}_0}{Z} = \frac{V_0}{\sqrt{R^2 + (\omega L)^2}} e^{i(\omega t - \pi/2 - \tan^{-1}(\omega L/R))}$$

$$\therefore \phi = \tan^{-1}(\omega L/R)$$

$$I_0 = B_0 \omega \pi a^2 / \sqrt{R^2 + (\omega L)^2}$$

$$c) \quad B_{\text{ind}} = \frac{\mu_0 I_0}{2R} = \frac{\mu_0}{2a} \frac{B_0 \omega \pi a^2}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t - \phi)$$

Problem 2 – Back EMF in Inductors

Consider the simple RL circuit shown in Figure 1. The purpose of the resistance R is to limit the current drawn from the AC source. Suppose you turn on the switch, which we assume is an ideal switch that can turn on and off instantaneously. The current starts flowing through the circuit and the back EMF produced by the inductor results in a slow growth of the current, $dI / dt = \mathcal{E}_0 / L$. Once the current reaches steady state ($dI / dt = 0$) you turn off the switch. We will approximate the “OFF” position by assuming a very high resistance value R_a across the terminals of the open switch, where the subscript a stands for air. Note that $R_a \gg R$. The sudden loss of current flow will result in a back EMF generated by the inductor.

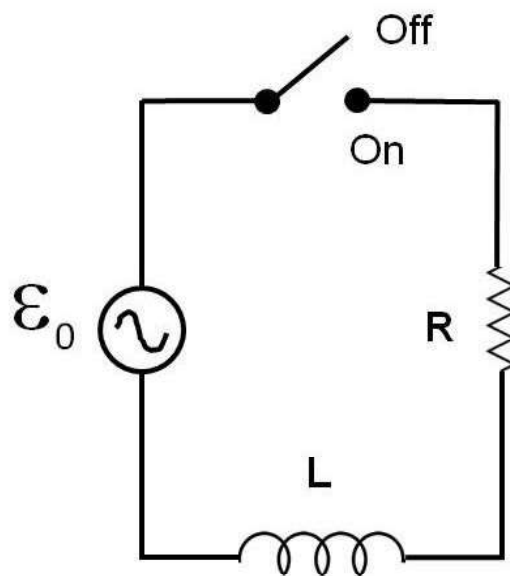


Figure 1: RL circuit with a switch.

- (a) Show that the current through the inductor dies down as $I(t) \approx I_0 e^{-tR_a/L}$, where I_0 is the current in the switch “ON” position. [1pt]
- (b) For the purpose of part (b) only, adopt the following specific values: $\mathcal{E}_0 = 110$ V, frequency $\omega/2\pi = 60$ Hz, $R = 100$ Ω , $L = 1$ mH and $R_a = 10^6$ Ω . Assume that the inductor can stand up to 10 kV of voltage across its input terminals. Compute the peak value of the back EMF across the inductor. You should find that the inductor burns up¹. [1pt]

¹ This experiment is not recommended!

- (c) Having been badly burnt by your first experiment, you come to appreciate the importance of reactance in circuits. Clearly, you need to cancel the reactance of the inductor so that huge back EMF is not generated. Relative to inductors, capacitors have a negative reactance. Keeping this in mind you devise the clever circuit shown in Figure 2 to limit the back EMF. In this circuit, R and L are as before² but you will have a choice in the value of C . Find the value of C , expressed in terms of R and L , that will result in zero reactance across terminals A and B. [1pt]

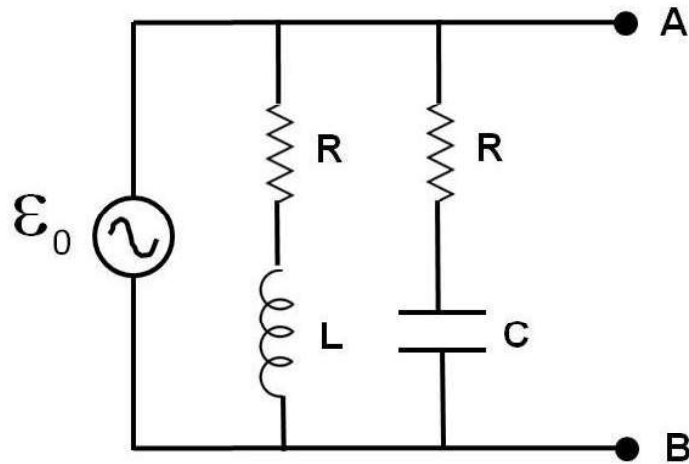


Figure 2

Use the value of C you found in part (c) in the following two parts.

- (d) Your goal is now to compute the time-averaged power dissipation in the circuit. In the first method, compute Z_R , the net resistive load across the terminals of the EMF source. Then find the average dissipated power knowing $\bar{P} = (1/2)\mathcal{E}_0^2/Z_R$. [1pt]
- (e) In the second method, compute the power dissipated across each resistive element and sum up to yield the total power dissipation. Compare the power values derived by the two methods. [Warning: this can be solved efficiently and rapidly with phasor algebra, provided you are aware of the nuances of phasor multiplication. The alternative approach is to use real functions but with care also]. [1pt]

² In parts (c), (d) and (e) we do NOT ascribe specific values to R , \mathcal{E}_0 and L like we did in part (b).

Problem 2 - Back EMF in Inductors

a [1pt]

As soon as the switch is turned on current starts to flow and application of Kirckoff's law yields

$$-L \frac{dI}{dt} + RI = \mathcal{E}_0$$

. Note that inductor opposed the action of turning on and produces an EMF to counteract the EMF of the supply. $I(0) = 0$ and so at early times we can ignore the RI term and find

$$\frac{dI}{dt} = \frac{\mathcal{E}_0}{L}$$

In steady state, the amplitude of the current flowing through this L - R circuit is easily computed (L and R are in series) and found to be

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + L^2\omega^2}}$$

For the specific value of $R = 100$ ohm, $\mathcal{E}_0 = 110$ V and $L = 1$ mH we find $I = 1.1$ A (dominated by the resistor).

Once the switch is turned off the resistance in the circuit is $R + R_a$ which is entirely dominated by R_a . The rms voltage drop across this resistor is IR_a (we can ignore the drop across R and the voltage provided by the source) which is approximately 1.1×10^6 V. This will surely blow up our inductor. Ignoring this physical discussion we have mathematically

$$L \frac{dI}{dt} + IR_a = 0$$

The boundary condition is $I(0) = I$ (with time zero being the time at which the switch was turned off). The rms current through the circuit decays as $I \exp(-\frac{t}{(L/R)})$. The time constant is small, 1 ns (whence, anticipating this situation, we invoked an ideal switch!).

b [1pt]

The impedance from the resistance and inductor is

$$Z_1 = R + iL\omega$$

whereas that from the resistance and capacitor is

$$Z_2 = R + \frac{1}{iC\omega}$$

The admittance across the terminal A and B is

$$\begin{aligned} Y &= \frac{1}{Z_1} + \frac{1}{Z_2} \\ &= \frac{1}{R + iL} + \frac{1}{R + \frac{1}{iC\omega}} \\ &= \frac{2R + iA}{B + iRA} \end{aligned}$$

where $A = L\omega - \frac{1}{C\omega}$ and $B = R^2 + L/C$. The impedance is

$$\begin{aligned} Z &= \frac{B + iRA}{2R + iA} \\ &= \frac{B + iRA}{2R + iA} \times \frac{2R - iA}{2R - iA} \\ &= \frac{2BR + RA^2 + iA(2R^2 - B)}{4R^2 + A^2} \\ &= Z_R + iZ_Y \end{aligned}$$

The reactance can be eliminated (i.e. set to zero) by choosing C so that $2R^2 = B$ leading the requirement

$$C = \frac{L}{R^2}$$

For this choice of C the resistance is

$$Z_R = \frac{R(4R^2 + A^2)}{4R^2 + A^2} = R$$

c [1pt]

The total current flowing out of the EMF source is

$$\mathcal{I} = \frac{\mathcal{E}_0}{Z} = \frac{\mathcal{E}_0}{R}$$

Note that the impedance is entirely resistive and thus the current is in phase with the EMF. The mean power is trivially found to be

$$\bar{P} = 1/2 \mathcal{E}_0 I_0 = \frac{\mathcal{E}_0^2}{R} \quad (1)$$

d [1pt]

Let I_1 and I_2 be the current through impedance Z_1 and Z_2 , respectively.

$$I_1 = \frac{\mathcal{E}_0}{Z_1} = \frac{\mathcal{E}_0}{R + i\omega L} = \frac{\mathcal{E}_0}{\sqrt{R^2 + L^2\omega^2}} = I_1 \exp(i\phi_1)$$

where $\tan \phi_1 = -L\omega/R$ and $I_1 = \mathcal{E}_0/\sqrt{R^2 + L^2\omega^2}$

We now compute I_2 and use the above equation to eliminate C :

$$I_2 = \frac{\mathcal{E}_0}{Z_2} = \frac{\mathcal{E}_0}{R + \frac{1}{iC\omega}} = \frac{\mathcal{E}_0(L\omega/R)}{\sqrt{R^2 + L^2\omega^2}} \exp(i\phi_2)$$

where $\tan \phi_2 = R/(L\omega)$

We now compute the dissipation across each of the two resistors using real functions and later with phases. The voltage drop across the resistor has the same phase as the current. Thus both current and voltage are the same form., $A \cos(\omega t + \phi)$ where A is the amplitude (say, A for current and $A_V = RA$ for the voltage) and ϕ is the phase. The time averaged dissipated power is $(1/2)A^2R$. The sum of the power dissipated across the two resistors is thus

$$\bar{P} = \frac{1}{2}(I_1^2 R + I_2^2 R) = \frac{1}{2} \frac{\mathcal{E}_0^2}{R} \quad (2)$$

which matches that found previously (equation 1).

We will now compute the dissipated power using phasor algebra. There is a subtle point here and that has to do with the phase algebra. The power dissipated across any element (resistor or otherwise) is not the product of the phasor (say, current and voltage) will result in a signal of the form $\exp(i2\omega t + \phi_I + \phi_V)$ where ϕ_I is the phase of the current and ϕ_V is the phases of the voltage. This is the most certainly not the work that has been across the element. The right expression is VI^* . For a resistance, $V = RI$ and thus the power dissipates is RII^* .

the time-averaged power dissipated in each resistor is

$$\bar{P}_1 = \frac{1}{2} I_1 I_2^* R = \frac{\mathcal{E}_0^2 R}{(R^2 + L^2 \omega^2)}$$

$$\bar{P}_2 = \frac{1}{2} I_2 I_2^* R = \frac{\mathcal{E}_0^2 (L\omega/R)^2 R}{(R^2 + L^2 \omega^2)}$$

the sum of which is the same as that found in equation 2.